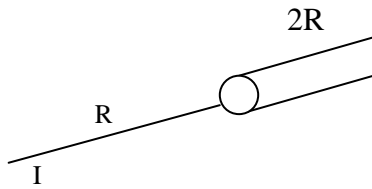


## Assignment 3



1) An instantaneous pulse with current  $I$  travels down a PCB line, which has an  $R$  ohm impedance and which connects to a  $2R$  ohm cable. What is the relation between the pulse with current  $I_2$  that continues down the higher impedance cable and the pulse with current  $I_1$  that reflects backward? Show derivation.

2) The resistivity of the  $2R$  line is twice that of the  $1R$  line. If the  $2R$  line cross sectional radius is twice that of the  $1R$  line cross sectional radius, what does that say about the current transmission loss on the  $1R$  line with respect to that on the  $2R$  line?

3) What is the octal and hexadecimal equivalent of decimal number 1022? Prove without using a calculator!

4) An OR is formed between the two outputs of the SR flip-flop resulting at point Z. What is the Boolean algebraic expression relating Z to inputs S and R. Use Q and  $\overline{NQ}$  as the outputs of the flip-flop.

5) An RC circuit is driven by power supply  $V_{cc}$ . Express the voltage  $V$  across the capacitor as a function of time  $t$  using  $R$  as the resistance and  $C$  as the capacitance of the circuit.