

Lecture 9/10: VHDL

VHDL => Very-high-speed-integrated-circuit Hardware Description Language

Developed for US Dept of Defense in 1983

Models IC design of target assembly board

Two kinds of design description: structural or behavioral

Strong emphasis on logic concurrency and timing

Uses standard set of libraries that describe design entities and constructs

Top-down design method employed: recursive partitioning of components into subcomponents

Subcomponents broken down into manageable design block VHDL description

Structural description: Instantiations of modules within other modules using signal identifiers

Behavioral description: Procedural statements that determine relationship between input and output signals

Entity declaration: describes interface of logical subcomponent/block

Architectural declaration: describes structural or behavioral operation of component

ENTITY latch IS

PORT(s, r : IN BIT; q, nq : OUT BIT);

END latch;

ARCHITECTURE dataflow OF latch IS

BEGIN

q <= r NOR nq;

nq <= s NOR q;

END dataflow;

SR LATCH

Use of COMPONENT or PORT MAP declarations can be used when subcomponents already defined.

PORT/PORT MAP declarations can also take array assignments using BIT_VECTOR and DOWNTO.

Examples:

```
(latch already defined above)
ARCHITECTURE structure OF latch IS
  COMPONENT nor_gate
    PORT( a, b: IN BIT; c: OUT BIT);
  END COMPONENT;
  BEGIN
    N1: nor_gate
      PORT MAP (r, nq, q);
    N2: nor_gate
      PORT MAP (s, q, nq);
  END structure;
```

```
2x1 4-line Multiplexer
ENTITY mux2 IS
  PORT( a: IN BIT_VECTOR(3 DOWNTO 0);
        b: IN BIT_VECTOR(3 DOWNTO 0);
        c: IN BIT;
        d: OUT BIT_VECTOR(3 DOWNTO 0));
  END mux2;
ARCHITECTURE mux2_arch OF mux2 IS
  BEGIN
    IF c = '0' THEN
      d <= a;
    ELSE
      d <= b;
    END IF;
  END mux2_arch;
```

Take case of serial_adder: components are full_adder, flip_flop, counter, and shifter:

How would you do component description of serial adder? Exercise: fill in PORT arguments.

Lecture 9/10: VHDL (cont.)

```
ENTITY serial_adder IS
  PORT (a, b, start, clock : IN BIT; ready: OUT BIT; result: BUFFER BIT_VECTOR(7 DOWNTO 0));
END serial_adder;
ARCHITECTURE structure OF serial_adder IS
  COMPONENT counter IS
    PORT(...);
  END COMPONENT;
  COMPONENT full_adder IS
    PORT(...);
  END COMPONENT;
  COMPONENT flip_flop IS
    PORT(...);
  END COMPONENT;
  COMPONENT shifter IS
    PORT(...);
  END COMPONENT;
END structure;
```

SIGNAL statement can also be used to make BIT/BIT_VECTOR assignments.
PROCESS statement is used to make VARIABLE declarations and sequential statements.

Example:

```
SIGNAL x: BIT_VECTOR (7 DOWNTO 0);
```

```
...
```

```
...
```

```
PROCESS (x)
```

```
  VARIABLE p : BIT;
```

```
BEGIN
```

```
  p = '0';
```

```
  FOR I IN 7 DOWNTO 0 LOOP ←===== can use NEXT statement also
```

```
    p = p XOR x(i);
```

```
  END LOOP; ←===== with NEXT WHEN <condition> here
```

```
END PROCESS;
```

WAIT UNTIL <condition> or EXIT WHEN <condition> statements can be used also inside LOOP.

Can use CASE <expression/condition> IS

```
  WHEN case1
```

```
  ...
```

```
  WHEN case2
```

```
  ...
```

```
END CASE;
```

```
*****
```

Exercise: Instead of structural component description of serial_adder, do its gory behavioral description.
Hint: don't segregate architecture statement into components.

```
*****
```

Functional simulation – models how design functions without timing reference



Timing simulation – model internal delays present in real-time circuits

Lecture 9/10: VHDL (cont.)



Inertial delay model – timing simulation using AFTER clause in signal assignment

Transport delay model – timing simulation using AFTER clause that triggers on ANY signal state change


Example:

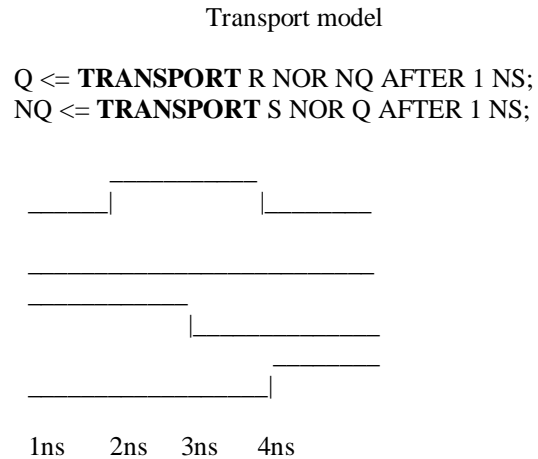 

But what if R pulse is < 1ns :

  

 Exercise: Now describe the following with VHDL.



```

ARCHITECTURE signals IS
    SIGNAL a,b : BIT;
BEGIN
    PROCESS
    BEGIN
        A <= '0', '1' AFTER 16 NS, '0' AFTER 24 NS;
        B <= '1', TRANSPORT NOT A AFTER 20 NS;
    END PROCESS;
END signals;
    
```

Can use subroutines in VHDL using PROCEDURE statement. Example:

```

PROCEDURE byte_to_int (ib:
IN BIT_VECTOR(7 DOWNT0 0); oi:
OUT INTEGER) IS
    oi = 0;
    BEGIN
        FOR i IN 0 TO 7 LOOP
            IF ib(i) = '1' THEN
                oi = oi + 2**i;
            END IF;
        END LOOP;
    END byte_to_int;
    
```

Exercise: use PROCEDURE statement in ARCHITECTURE signals to get same result for B using A as input.